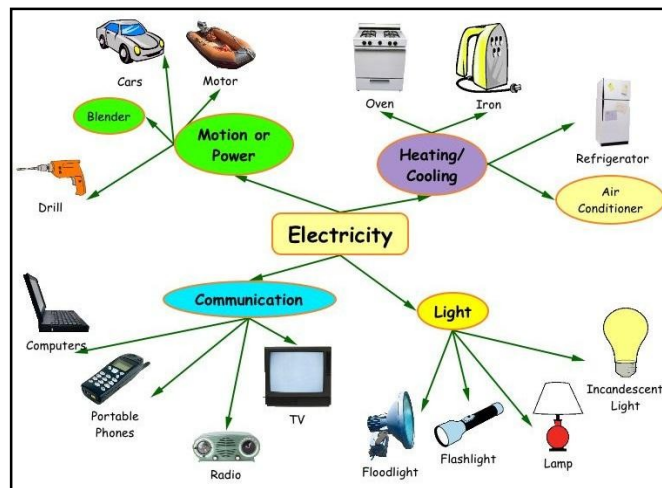


SCIENCE

Electricity and Circuits


- Electricity is an important source of energy.
- We get electricity from sources such as wind energy, solar energy, mechanical energy of water, nuclear energy, heat energy and chemical energy.
- Lights, fans, motors, radios, television, computers etc. are some common appliances which work on electricity.



- Electricity is provided by a powerstation.

Electric Cell

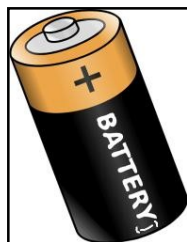
- An electric cell provides electricity to various devices in which electricity cannot be supplied directly.



- It consists of two terminals:
 - Positive terminal with a metal cap.
 - Negative terminal with a metal disc.
- A chemical is present in the cell which helps to produce electricity.
- Electricity to a bulb is provided by an electric cell.
- A bulb consists of two terminals:
 - A filament inside the bulb is a spirally wound wire which is supported by two thick wires at its ends.
 - An electrical cell is connected to the terminals of the bulb so that electricity from the cell can pass through it.
 - This electricity makes the filament in the bulb glow and thus emit light.
 - Electric cells are also used in alarm clocks, wristwatches, transistor radios, cameras and many other devices.

Electric Circuit

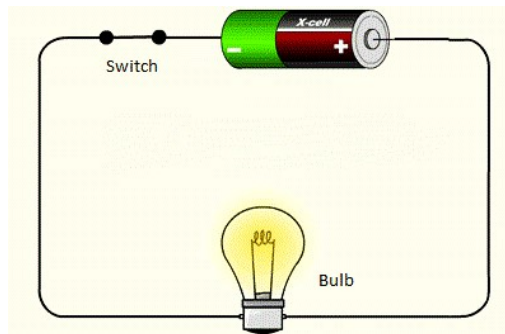
- An electric circuit consists of a complete path for electricity to pass.
- The simplest form of a circuit is when two terminals of a cell are connected to the two terminals of a bulb and a switch.



- When the terminals of the bulb are connected with the electric cell by wires, the current passes through the filament of the bulb making it glow.
- The direction of current flow is from the positive terminal to the negative terminal of the electric cell.

Electric Switch

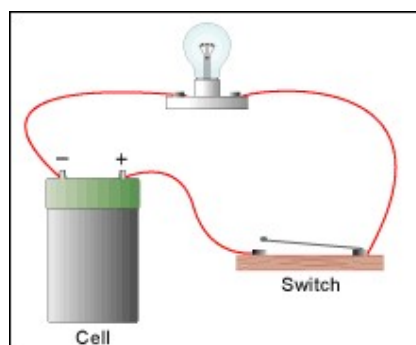- A device used to stop the flow of electricity by breaking the circuit is called a **switch**.




- A switch may be directly manipulated by a human as a control signal to a system, such as a computer's keyboard button, or to control power flow in a circuit, a light switch.
- Switches have different applications:
 - Toggle switches: Used in our houses.



- Pushbutton switches: Used in the starter of a water pump and in an engine.



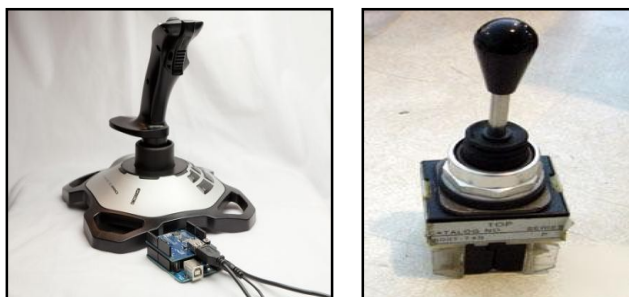- Joystick switches: Used in the remote control unit of a toy car.



Electric Conductors and Insulators

Conductors

- Materials which allow electricity to pass through them are called conductors.
- Metals are good conductors of electricity.
- Electric wires are made of metals which act as conducting materials, and are therefore used to make electrical circuits.

Insulators

- Materials which do not allow electricity to pass through them are called **insulators**.
- Insulators oppose electric current, and are therefore used as **protection** from the dangerous effects of electricity.
- **Water** is a **good conductor** of electricity. However, in its purest form i.e. **distilled water**, it acts as an insulator and is used in batteries.